

Frequency Shift Keying (FSK)


DUNCAN WOOD

ENCE 4110

11/12/2025



Introduction

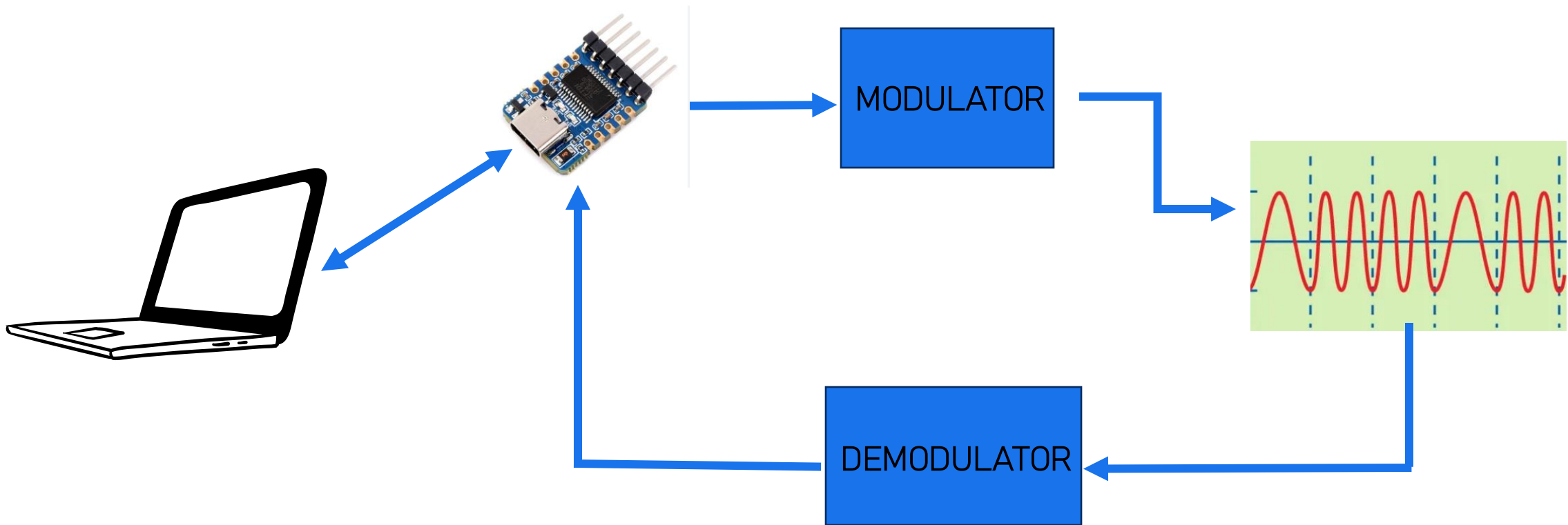Problem: Convert UART data into modulated FSK signal and send it back to the PC demodulated




What is Frequency Shift Keying?

 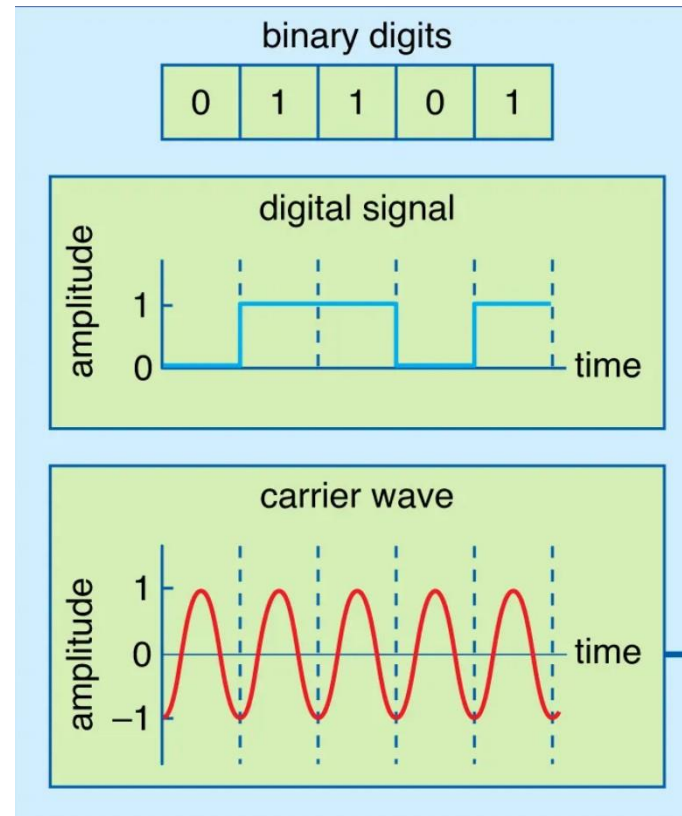
- FSK is a digital modulation technique widely used in modern technology.
- Bluetooth, digital radios, remotes.
- The digital counterpart of Frequency Modulation (FM)



 © 2006 The Authors
Journal compilation © 2006 Blackwell Publishing Ltd




System Overview

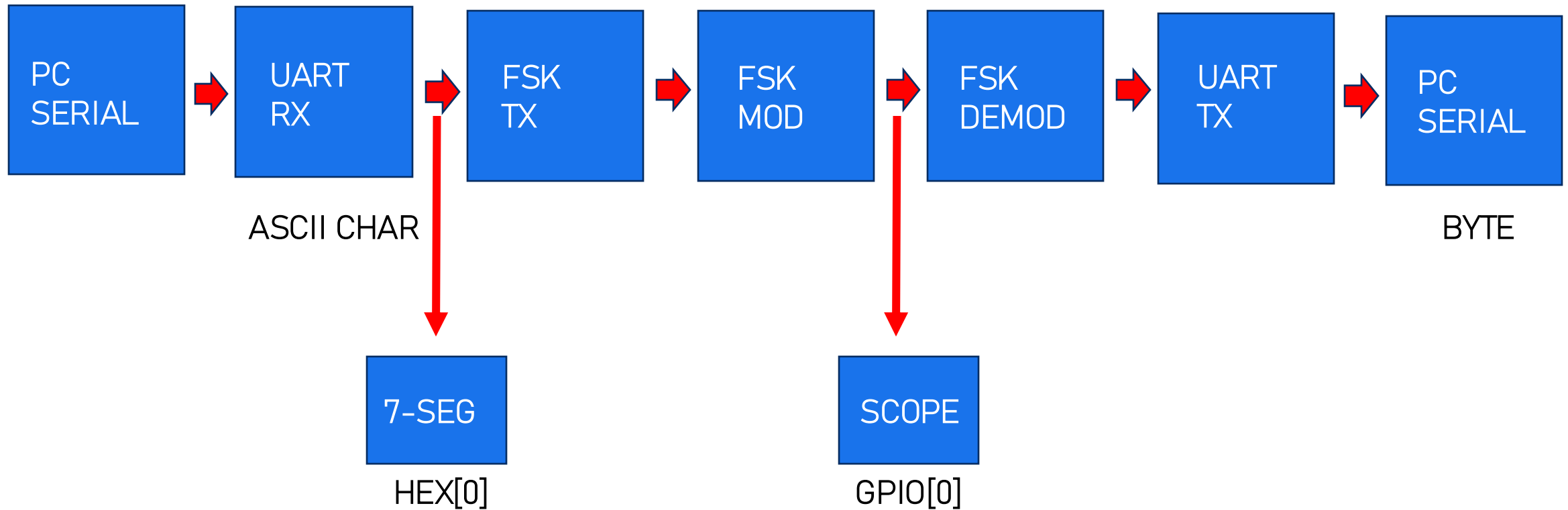



FSK Transmit FSM

 - Serializes byte into 10-bit frame (start, data, stop)
- Holds each bit for defined number of clock cycles; the symbol period.
- Synchronizes the UART data with the FSK modulator.




Symbol Timing

  - UART Baud: 115200
- FPGA Clock: 50 MHz
- Clocks per symbol = $50\text{e}6 / 115200 \approx 434$
- One bit = 434 clock cycles \rightarrow one full tone interval




FSK Modulator

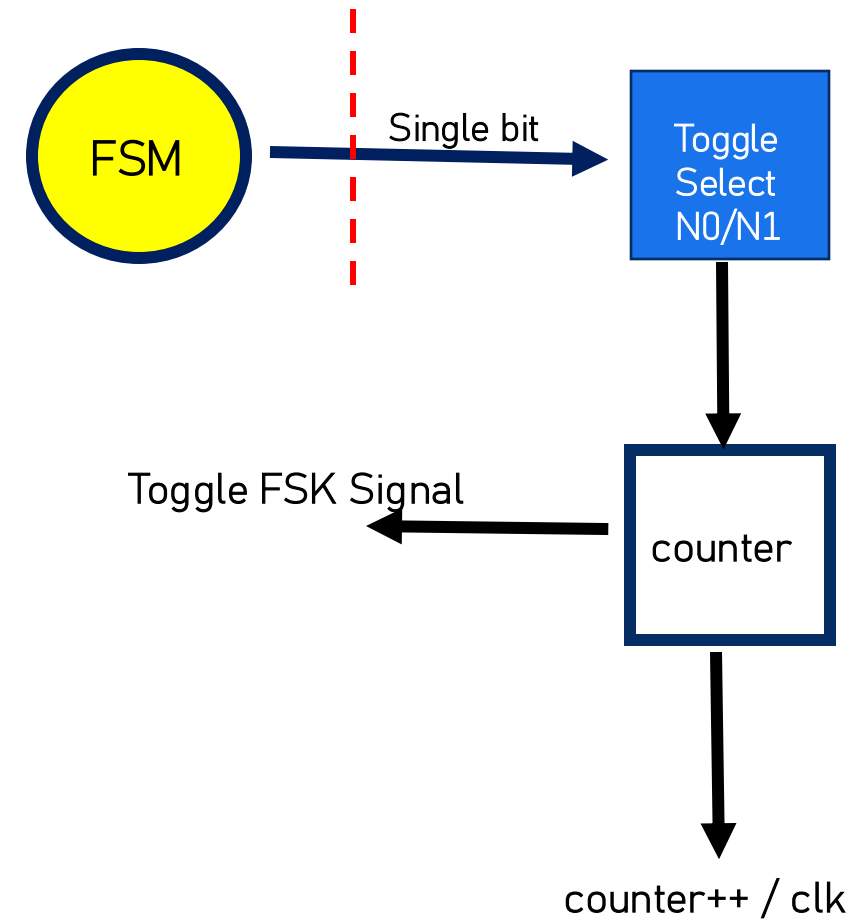- Simple toggle-counter structure:
 - Counter resets when reaching N_0/N_1
 - Output bit flips on reset \rightarrow square wave
- Frequency
 - $f=1/(2 \times N)$
 - If bit==1 use **N1** (shorter interval \rightarrow higher frequency).
 - If bit==0 use **N0** (longer interval \rightarrow lower frequency).



FSK Demodulator

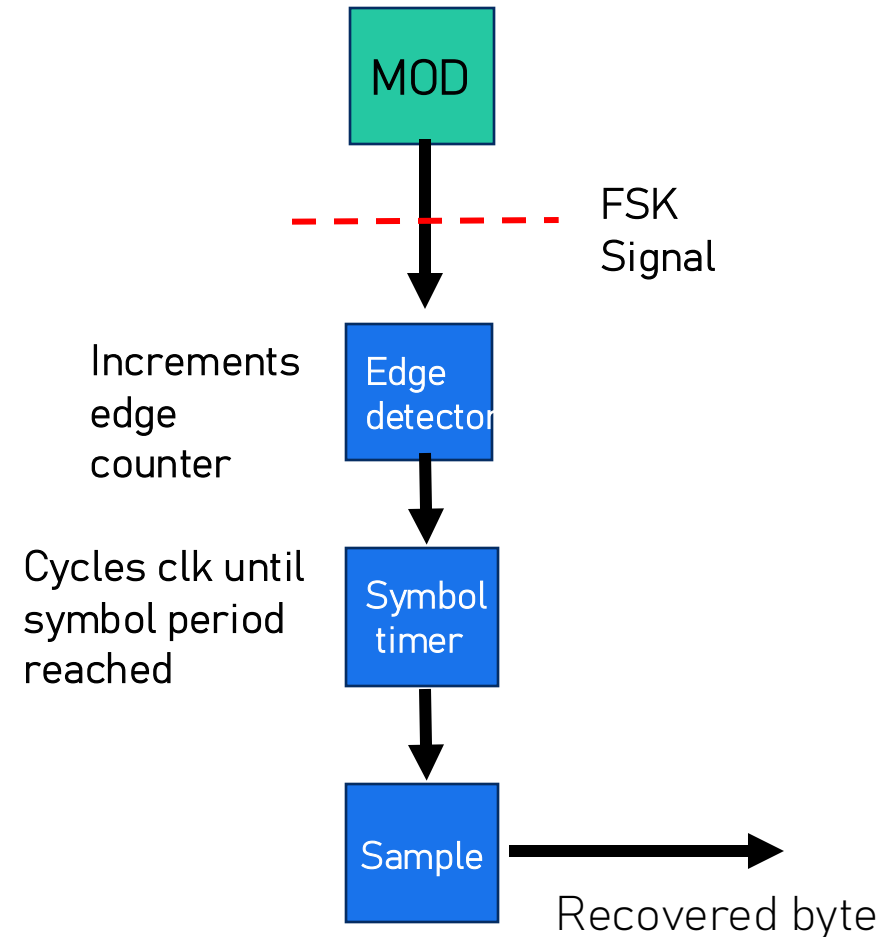- Edge-counting demodulator:
 - Detect transitions of **fsk_in**
 - Count edges per symbol window (434 clocks)
 - Compare to threshold (~20 edges)
- Decision rule:
 - More edges → high tone → bit = 1
 - Fewer edges → low tone → bit = 0
- Reassemble bits into bytes






UART Transmitter / Receiver



- Receive and transmit the input and output message of the FSK logic.

Testing and Verification

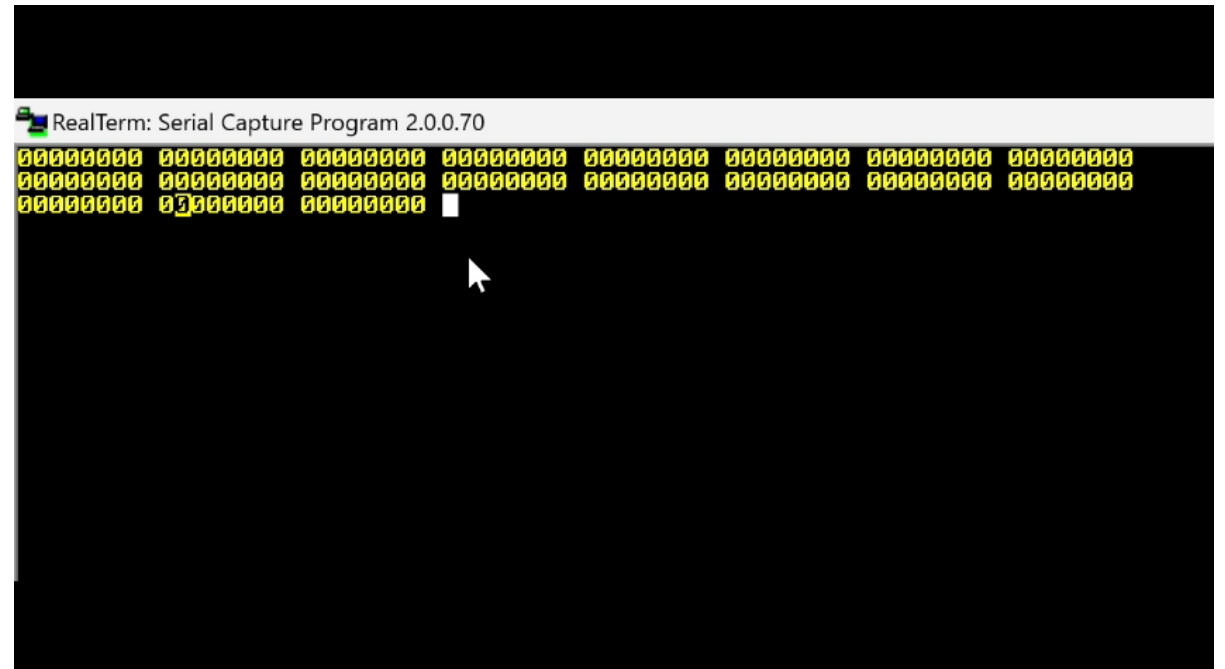 

 

RealTerm: Serial Capture Program 2.0.0.70

00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000
00000000	00000000	00000000	00000000				

Future Work

Problem Observed

- Characters echoed from the demodulator do not match the UART key pressed
- Indicates bit or symbol misalignment between transmitter and receiver timing.

Likely causes

- **Symbol boundary drift** — demodulator's 434-clock window may start mid-symbol
- **Threshold sensitivity** — fixed midpoint (≈ 20 edges) may misclassify noisy or marginal tones.
- **Byte framing ambiguity** — demodulator doesn't yet detect start/stop bits; it simply groups 8 bits sequentially.

Possible Solution: add protocol layer and additional synchronizer to implement start/stop validation.

Conclusions

- Built a complete digital FSK modem on FPGA.
- Demonstrated real-time chain:
 - UART RX → FSK TX FSM → Modulator →
Demodulator → UART TX

Key Insights

- Timing precision is key for symbol alignment
- Simple edge count demodulation works conceptually but lacks robustness.

